

Homework 3 – C++ RT-level Design and Modeling

Taghizadeh,
810198373

I. INTRODUCTION

In this homework, we are about to make a 64-bit Adder from a 4-bit Adder. The algorithm is to split inputs into 16 packets of 4 bits and in 16 clock cycles, add each packet of inputs. So in the each cycle 4 bits of the *sum* output will be calculated. Carry out of the each addition of the 4-bits packets is used as carry in of the next partial addition. By repeating this about 16 times, the entire *sum* output and carry out will be calculated.

II. HOMEWORK PARTS REPORT

A. 64-bit Adder's Data Path Schematic

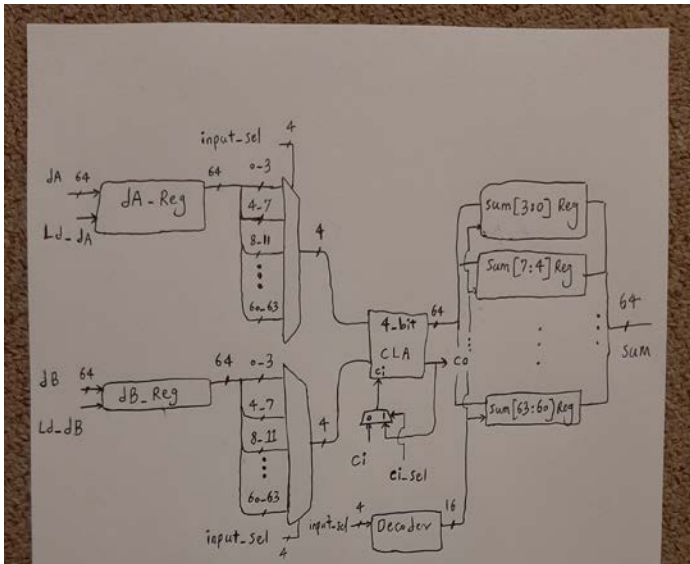


Fig. 1 64-bit Adder Data Path Schematic

B. 64-bit Adder's Data Path in C++

First by the *range()* method of the *bus* class, 4 bits of *a* and *b* inputs are selected by the *internal_4_bits_adder_inputs_selector* to added by the internal 4-bit adder. At first the carry in of the internal 4-bit adder is equal to the carry in of the 64-bit adder. Then in the next cycles, the carry in of the internal 4-bit adder will be equal to the carry out of the previous addition which is selected by the *internal_4_bits_adder_ci_selector* signal. After addition, 4 bits of the *sum* output of the 64-bit adder is ready. So by the *fill_given_range()* method of the *bus* method,

4 bits of the *sum* output will be filled by the sum result of the current addition.

```
5 class Adder_64_bits_DataPath{
6     bus *a, *b;
7     bus *ci;
8     bus *internal_4_bits_adder_inputs_selector;
9     bus *internal_4_bits_adder_ci_selector;
10    bus *co;
11    bus *sum;
12    public:
13        Adder_64_bits_DataPath(bus& a, bus& b, bus& ci, bus&
            internal_4_bits_adder_inputs_selector, bus&
            internal_4_bits_adder_ci_selector, bus& co, bus& sum);
14        void evl ();
15};
16
```

Fig. 2 64-bit Adder Data Path Declaration

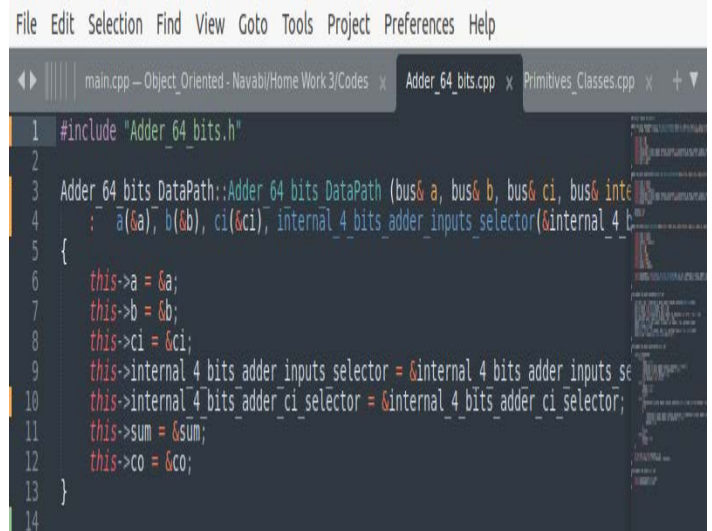


Fig. 3 64-bit Adder Data Path Constructor

```

55 void fill_given_range(int begin_index, int end_index, string s)
56 {
57     int end = v.length() - 1 - begin_index;
58     int begin = v.length() - 1 - end_index;
59     for(int i = begin; i <= end; i++)
60         v.at(i) = s.at(i - begin);
61 }
62
63 string get_bus_values()
64 {
65     return v;
66 }
67
68 int to_uint()
69 {
70     int res = 0;
71     for(int i = 0; i < v.length(); i++){
72         if(v.at(i) == '1')
73             res += int(pow(2, v.length() - 1 -
74 i));
75     }
76     return res;
77 }

```

Fig. 4 64-bit Adder Data Path Utility Bus Methods

```

45 void Adder_64_bits_DataPath::evl ()
46 {
47     int sel = (4 * internal_4_bits_adder_inputs_selector->to_uint());
48     bus a_input = a->range(sel, sel + 3);
49     bus b_input = b->range(sel, sel + 3);
50     bus ci_input = (*internal_4_bits_adder_ci_selector == "0") ? *ci : *co;
51     bus partial_sum = sum->range(sel, sel + 3);
52     Adder_4_bits(a_input, b_input, ci_input, *co, partial_sum);
53     adder_4_bits.evl();
54     sum->fill_given_range(sel, sel + 3, partial_sum.get_bus_values());
55 }
56

```

Fig. 5 64-bit Adder Data Path Evaluation Method

D. 64-bit Adder's Controller in C++

In the first state, *internal_4_bits_adder_inputs_selector*, *internal_4_bits_adder_ci_selector*, are initialized by 0. If the *start* signal is asserted we will go to the next state, else we will stay on the first state and the *done* signal will remain 1. In the second state the *done* signal is deactivated. In the final state *internal_4_bits_adder_inputs_selector* is increased. This state will be repeated about 16 times to calculate all 4 packets of the *sum* output. By the end of these repetitions the *sum* output will be calculated, so the *done* signal is asserted and we will get back to the first state. During the final state the *internal_4_bits_adder_ci_selector* signal will remain 1 to cascade the carry out of each partial addition to the carry in of the next partial addition to calculate the *sum* output correctly.

```

17 class Adder_64_bits_Controller{
18     bus *rst;
19     bus *clk;
20     bus *start;
21     bus *done;
22     bus *internal_4_bits_adder_inputs_selector;
23     bus *internal_4_bits_adder_ci_selector;
24     int Nstate, Pstate;
25 public:
26     Adder_64_bits_Controller(bus& rst, bus& clk, bus& start,
27         bus& internal_4_bits_adder_inputs_selector, bus&
28         internal_4_bits_adder_ci_selector, bus& done);
29     void evl ();
30 };

```

Fig. 7 64-bit Adder Controller Declaration

C. 64-bit Adder's Controller Schematic

 


Fig. 6 64-bit Adder Controller Schematic

```

15 Adder_64_bits_Controller::Adder_64_bits_Controller (bus& rst, bus& clk, bus& start
16 {
17     this->rst = &rst;
18     this->clk = &clk;
19     this->start = &start;
20     this->internal_4_bits_adder_inputs_selector = &internal_4_bits_adder_inputs_se
21     this->internal_4_bits_adder_ci_selector = &internal_4_bits_adder_ci_selector;
22     this->done = &done;
23
24     Nstate = 0;
25     Pstate = 0;
26 }
27

```

Fig. 8 64-bit Adder Controller Constructor

```
File Edit Selection Find View Go Tools Project Preferences Help
main.cpp — Object_Oriented - Navabi/Home Work 3/Codes x Adder_64_bits.cpp x Primitives_Classes.cpp x
37
38 void Adder_64_bits Controller::evl ()
39 {
40     switch (Pstate){
41     case 0:
42         *done = "1";
43         *internal_4_bits_adder_inputs_selector = "0000";
44         *internal_4_bits_adder_ci_selector = "0";
45         if(*start == "1") Nstate = 1;
46         else Nstate = 0; break;
47     case 1:
48         *done = "0";
49         Nstate = 2;
50         break;
51     case 2:
52         if(internal_4_bits_adder_inputs_selector->to_uint() == 17) Nstate = 0;
53         else
54         {
55             *internal_4_bits_adder_inputs_selector = *internal_4_bits_adder_in
56             *internal_4_bits_adder_ci_selector = "1";
57             Nstate = 2;
58         }
59         break;
60     default:
61         Pstate = 0;
62         break;
63     }
64
65     if (*rst == "1") Pstate = 0;
66     else if (*clk == "P") Pstate = Nstate;
67 }
68
```

E. 64-bit Adder's Top Level in C++

```

30 class Adder_64_bits{
31     Adder_64_bits_DataPath *DataPath;
32     Adder_64_bits_Controller *Controller;
33     bus *rst, *clk;
34     bus *start;
35     bus *a, *b;
36     bus *ci;
37     bus internal_4_bits_adder_inputs_selector;
38     bus internal_4_bits_adder_ci_selector;
39     bus *co;
40     bus *sum;
41     bus *done;
42     public:
43         Adder_64_bits(bus& rst, bus& clk, bus& start, bus& a, bus&
b, bus& ci, bus& co, bus& sum, bus& done);
44
45         void set_rst(bus *given_rst) { rst = given_rst; };
46         void set_clk(bus *given_clk) { clk = given_clk; };
47         void set_start(bus *given_start) { start = given_start; };
48
49         void evl ();
50 };

```

```
File Edit View Go Tools Project Preferences Help
main.cpp — Object_Oriented - Navabi/Home Work 3/Codes x Adder_64_bits.cpp x Primitives_Classes.cpp x + v
21
28 Adder_64_bits::Adder_64_bits (bus& rst, bus& clk, bus& start, bus& a, bus& b, bus& ci)
29 {
30     this->rst = &rst;
31     this->clk = &clk;
32     this->start = &start;
33     this->a = &a;
34     this->b = &b;
35     this->ci = &ci;
36     this->co = &co;
37     this->sum = &sum;
38     this->done = &done;
39
40     this->DataPath = new Adder_64_bits_DataPath(a, b, ci, internal_4_bits_adder_in
41     this->Controller = new Adder_64_bits_Controller(rst, clk, start, internal_4_bi
42
43 }
44
```

```
89 void Adder_64_bits::evl ()
90 {
91     this->Controller->evl();
92     this->DataPath->evl();
93 }
```

Line 93, Column 2

Tab Size: 4 C++

F. 64-bit Adder Test Bench

[illegible]

